

# JOIN



Telegram  
@PuneEngineers

For more Subjects

<https://www.studymedia.in/fe/notes>



**CLICK HERE**  
@PuneEngineers



SCAN ME




## Behaviour of a Pure Resistor in an AC Ckt.:

Consider a pure resistor  $R$  connected across an alternating voltage source  $V$  as shown in figure.

Let, the alternating voltage be;

$$V = V_m \sin \omega t \quad (1)$$

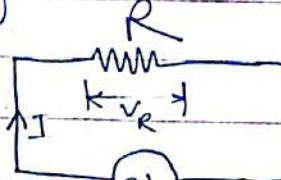Current:  $I = \frac{V}{R} = \frac{V_m \sin \omega t}{R}$



$$\Rightarrow I = I_m \sin \omega t \quad (2)$$

$$V = V_m \sin \omega t$$

$$\therefore V_m/R = I_m$$

where;  $I_m$  = max<sup>m</sup> value of alternating current.  
From equ<sup>n</sup> (1) & (2); it is clear that the current is in phase with Vtg. in a purely resistive ckt.

Waveform:-

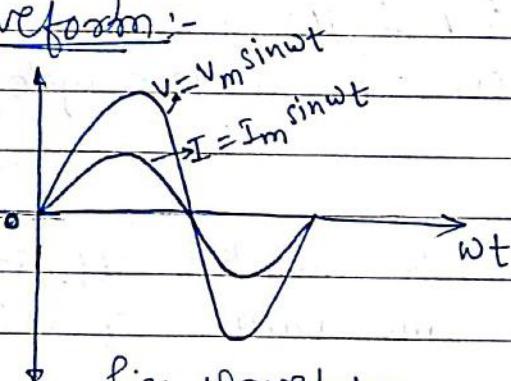


fig:- Waveform

Phasor Diagram:-

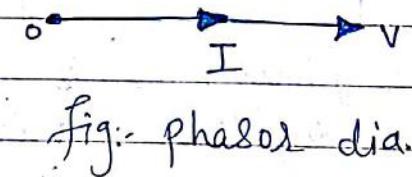


fig:- phasor dia.

Impedance:- It is the resistance offered ~~to~~ to the flow of current in an ac ckt. In purely resistive circuit;

$$Z = \frac{V}{I} = \frac{V_m \sin \omega t}{I_m \sin \omega t} = \frac{V_m}{I_m} = R$$

Phase Difference:- from equ<sup>n</sup> (1) & (2); the Vtg & current are in phase with each other, the phase difference is zero

$$\phi = 0^\circ$$

Powerfactor :- It is defined as the cosine angle b/w the Vtg & current phasors.

$$\therefore \text{powerfactor} = \cos \phi = \cos(0^\circ) = 1$$

Power :- The instantaneous power is given by;


$$P = V \cdot I$$

$$= V_m \sin \omega t \cdot I_m \sin \omega t$$

$$= V_m I_m \sin^2 \omega t$$

$$= V_m I_m \left( \frac{1 - \cos 2\omega t}{2} \right) = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$
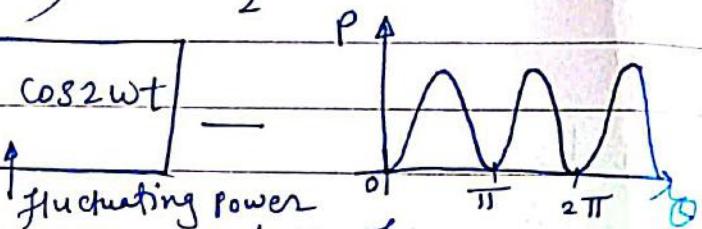
$$\boxed{P = \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t}$$



② Average power :-

$$P_{avg} = \frac{V_m I_m}{2} - 0 \quad \because \text{The fluctuating power}$$

↑ freq of

is twice the applied Vtg  
freq. & its average value  
over a complete cycle is zero.

$$P_{avg} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$\boxed{P_{avg} = \frac{V \cdot I}{rms \cdot rms}}$$


∴ Thus; Power in a purely resistive ckt. is equal to the product of rms values of voltage and current.

## Behaviour of a Pure Inductor in an AC Ckt.

consider; a pure inductor

L connected across an alternating vtg (V) as

shown in fig.

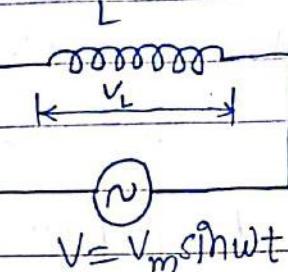

Let; the alternating vtg be;

$$V = V_m \sin \omega t \quad \text{--- (1)}$$

Current:

The alternating current is given by;

$$i = \frac{1}{L} \int V \cdot dt = \frac{1}{L} \int V_m \sin \omega t \cdot dt$$

$$= \frac{V_m}{\omega L} (-\cos \omega t)$$

$$= \frac{V_m}{\omega L} \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$i = I_m \sin \left( \omega t - \frac{\pi}{2} \right) \quad \therefore I_m = \frac{V_m}{\omega L} \quad \text{--- (2)}$$

where;  $I_m = \text{max}^m$  value of an alternating current.

From eqn ① & ②; it is clear that the current lags behind the vtg by  $90^\circ$  in a purely inductive ckt.

Waveform:-

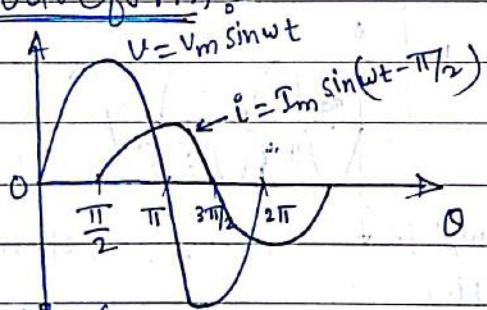


fig:- waveform

Phasor diagram:-

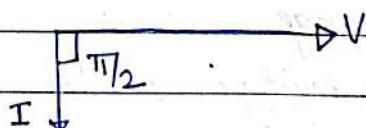


fig:- phasor dia.

Impedance:- In a purely inductive ckt;

$$Z = \frac{V}{I} = \frac{V_m}{I_m} = \frac{V_m}{\frac{V_m}{\omega L}} = \omega L$$

$$Z = \omega L$$

where;  $WL$  - is called inductive reactance  
 & it is denoted by  $X_L$  & its unit is  $\Omega$

$$X_L = \omega L = 2\pi f L$$

a) if dc supply  $f=0$   $X_L=0$

thus; inductor acts as a short-circuit for a dc supply.

Phase difference:-

It is the angle b/w the voltage & current phasors.

$$\phi = 90^\circ$$

Power factor:- It is defined as the angle b/w voltage & current phasors

$$P.F. = \cos \phi = \cos(90^\circ) = 0$$

Power:- a) Instantaneous power is given by;


$$P = V \cdot I$$

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t - \frac{\pi}{2})$$

$$P = -V_m I_m \sin \omega t \cdot \cos \omega t \quad \because \sin(\omega t - \frac{\pi}{2}) = -\cos \omega t$$

$$P = -\frac{V_m I_m}{2} \sin 2\omega t \quad \because \sin \omega t \cdot \cos \omega t = \frac{1}{2} \sin 2\omega t$$
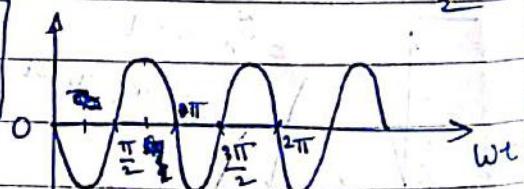
$$P = -\frac{V_m I_m}{2} \sin 2\omega t$$



b) Average power:-

Average power for one complete cycle is zero (becoz, the freq is doubled).

$$P_{avg} = 0$$

Hence; Power Consumed by a purely inductive ckt. is zero.

## Behaviour of a Pure Capacitor in an AC Ckt. :-

Consider; a pure capacitor  $C$


Connected across an alter-

nating vltg. ( $V$ ) as shown

in figure.

Let; the alternating vltg.

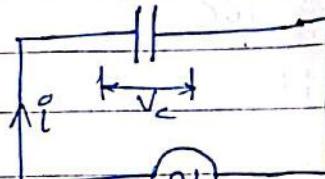is given by;  $V = V_m \sin \omega t$  — (1)



$$V = V_m \sin \omega t$$

current:- The alternating current is given by;

$$i = C \frac{dv}{dt} = C \frac{d}{dt} (V_m \sin \omega t)$$

$$= C V_m \cos \omega t (\omega) = \omega C V_m \cos \omega t$$

$$= \omega C V_m \sin (\omega t + \pi/2)$$

$$\boxed{i = I_m \sin (\omega t + \pi/2)} \quad (2)$$

$$\therefore I_m = \omega C V_m$$

where;  $I_m = \text{max}^m$  value of an alternating current.

From equ<sup>n</sup> (1) & (2); it is clear that the current leads the vltg by  $90^\circ$  in a purely capacitive ckt.

waveform :-

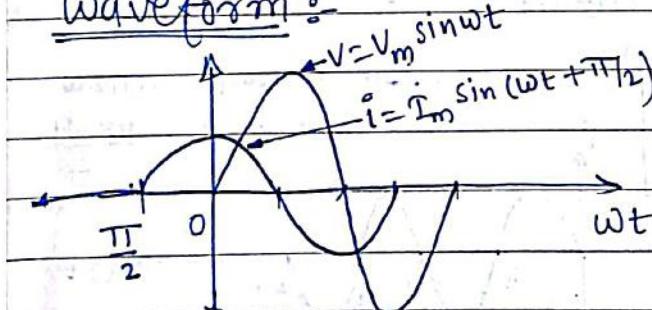


fig:- waveform

phasor dia. :-

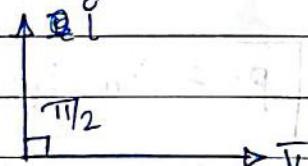


fig:- phasor dia

Impedance :- In a purely capacitive ckt;

$$Z = \frac{V}{I} = \frac{V_m}{I_m} = \frac{V_m}{\omega C V_m} = \frac{1}{\omega C}$$

$$\boxed{Z = \frac{1}{\omega C}}$$

where;  $\frac{1}{\omega C}$  is called Capacitive reactance.

& it is denoted by  $X_C$  & measured in  $\Omega$ .

$$Z = X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

(a) for dc supply  $f=0$   $X_C = \infty$

Hence, the capacitor acts as an open circ. for a dc supply.

Phase difference :-

It is the angle b/w the voltage & current phasors.

$$\phi = 90^\circ$$

Power factor :- It is defined as the cosine angle b/w voltage & current phasors.

$$P.F. = \cos \phi = \cos(90^\circ) = 0$$

Power :- (a) The instantaneous power is given by;

$$P = V \cdot I$$


$$= V_m \sin \omega t \cdot I_m \sin(\omega t + \pi/2)$$

$$= V_m I_m \sin \omega t \cdot \cos \omega t \quad \therefore \sin(\omega t + \pi/2) = \cos \omega t$$

$$P = \frac{V_m I_m}{2} \sin 2\omega t$$

$$\therefore 2 \sin \omega t \cos \omega t = \sin 2\omega t$$
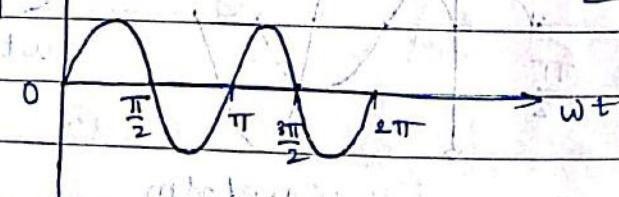
$$\sin \omega t \cos \omega t = \frac{\sin 2\omega t}{2}$$



(b) Average Power :- The average power for one complete cycle is zero. (becoz; freq is doubled).

$$P_{avg} = 0$$

Hence; power consumed by purely capacitive circ. is zero.

## Series R-L Ckt. :-

Figure shows a pure resistor ( $R$ ) connected in series with a pure inductor ( $L$ ) across an alternating voltage ( $V$ ).

In series with a pure inductor ( $L$ ) across an alternating voltage ( $V$ ).


Fig: series R-L ckt.

Let;  $V_{rms}$  &  $I_{rms}$  - be the rms value of applied voltage and current.


$\therefore$  Potential difference =  $V_R = R \cdot I$   
across  $R$

$\therefore$  Potential difference =  $V_L = X_L \cdot I$   
across  $L$

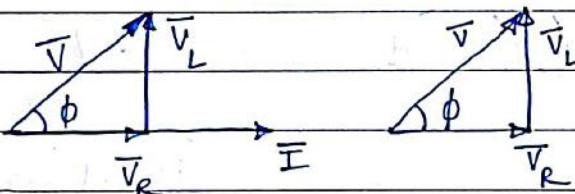$\therefore$  The  $\bar{V}_R$  is in phase with current  $\bar{I}$  whereas the voltage  $\bar{V}_L$  leads the current  $\bar{I}$  by  $90^\circ$ .



fig(a):- phasor dia

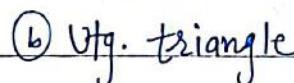

$$\cos \phi = \frac{V_R}{V}$$

Impedance :-

$$\bar{V} = \bar{V}_R + \bar{V}_L$$

$$= R \cdot \bar{I} + j X_L \cdot \bar{I}$$

$$\bar{V} = \bar{I} (R + j X_L)$$

$$\Rightarrow \boxed{\frac{\bar{V}}{\bar{I}} = R + j X_L = Z}$$

$$\bar{Z} = Z \angle \phi \quad \text{where; } Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + \omega^2 L^2}$$

$$\phi = \tan^{-1}\left(\frac{X_L}{R}\right) = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

Where;  $Z$  - Complex Impedance of R-L ckt.

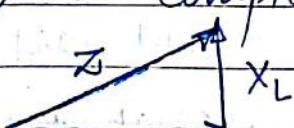


fig:- Impedance triangle

$$\cos \phi = \frac{R}{Z}$$

Current :- From phasor diagram, it is clear that the current ( $I$ ) lags behind the Vtg ( $V$ ) by angle ( $\phi$ ).

If the applied Vtg. is given by;

$$V = V_m \sin \omega t$$

then the current eqn will be;

$$I = I_m \sin(\omega t - \phi)$$

where;  $I_m = \frac{V_m}{Z}$

$$\& \phi = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

Waveform :-

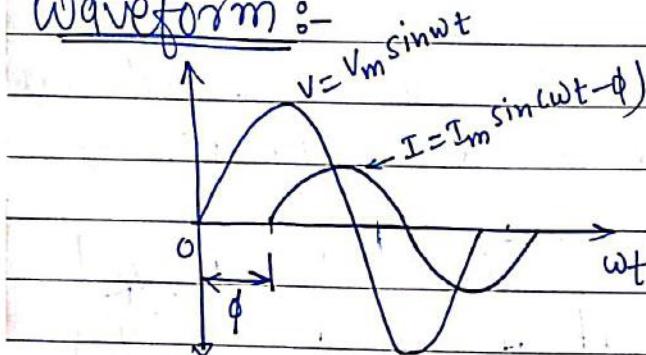


fig:- waveform

phasor dia:-

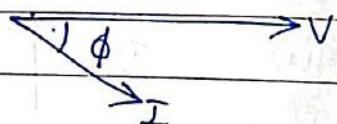


fig:- phasor dia

Power:-

(a) Instantaneous power

$$P = V \cdot I$$

$$= V_m \sin \omega t \cdot I_m \sin(\omega t - \phi)$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t - \phi) \quad \text{--- } \sin A \cdot \sin B$$

$$P = V_m I_m \frac{1}{2} \{ \cos \phi - \cos(2\omega t - \phi) \} = \frac{1}{2} \{ \cos(A+B) - \cos(A-B) \}$$

$$P = \frac{V_m I_m \cos \phi}{2} - \frac{V_m I_m \cos(2\omega t - \phi)}{2}$$

Constant  
power

fluctuating power

Thus; Power consists of a constant part ( $\frac{V_m I_m \cos \phi}{2}$ ) & a fluctuating power ( $\frac{V_m I_m \cos(2\omega t - \phi)}{2}$ ).

∴ The frequency of the fluctuating part is twice the applied vfg freq & its average value over one complete cycle is zero.

### (b) Average Power:

$$P_{avg} = \frac{V_m I_m \cos\phi}{2}$$

$$P_{avg} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos\phi$$

$$P_{avg.} = V_{rms} I_{rms} \cos\phi \quad \text{--- (1)}$$

The average power ( $P$ ) is dependent on the  $\text{In-phase component}$  of the current.

The average power is also called as Active Power & is measured in watt.

We know that a pure inductor & capacitor consume no power becoz all the power received from the source in a half cycle is returned to the source in the next half cycle. This circulating power is called reactive power.

Reactive power is the product of  $vfg$  & ~~current~~ reactive component of the current i.e.  $I \sin\phi$  and is measured in VAR (volt-ampere-reactive).

$$\therefore \text{Reactive Power } Q = VI \sin\phi \quad \text{--- (2)}$$


∴ The product of  $vfg$  & current is known as apparent power (S) and is measured in VA (volt-Amp).

$$S = \sqrt{P^2 + Q^2} \quad \text{--- (3)}$$

Power triangle:

In terms of ckt. components

$$\cos\phi = R/Z$$

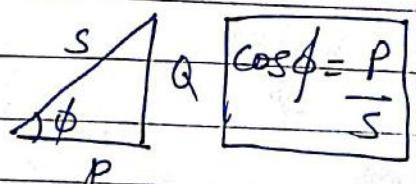

and  $V = Z \cdot I$

$$\therefore P = VI \cos \phi = ZI \cdot I \cdot \frac{R}{Z} = I^2 R$$

$$\therefore Q = VI \sin \phi = ZI \cdot I \cdot \frac{X_L}{Z} = I^2 X_L$$

$$\therefore S = VI = ZI \cdot I = I^2 Z$$

Power factor :- It is defined as the cosine angle b/w the  $\text{Vtg}$  & current phasors.

$$\text{Power factor} = \cos \phi$$

$$\therefore \text{from Vtg triangle} \Rightarrow \text{Pf} = \frac{V_R}{V}$$


$$\therefore \text{from Impedance triangle} \Rightarrow \text{Pf} = \frac{R}{Z}$$

$$\therefore \text{from Power triangle} \Rightarrow \text{Pf} = \frac{P}{S}$$

In case of an R-L series ckt., the pf. is lagging in nature.

## Series R-C Ckt.:-

figure shows a pure Resistor ( $R$ ) connected in series with a pure capacitor ( $C$ ) across an alternating vfg ( $V$ ).

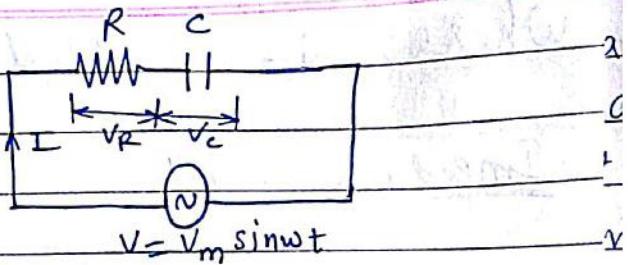

Let;  $V_{rms}$  &  $I_{rms}$  - be the rms value of applied vfg & c/n respectively.

$$\therefore \text{potential diff.} - v_R = RI$$

across R


$$\therefore \text{potential diff.} - v_C = X_C I$$

across C


$\therefore$  The vfg  $\bar{v}_R$  is in phase with current ( $\bar{I}$ ) whereas  $\bar{v}_C$  lags behind the current ( $\bar{I}$ ) by  $90^\circ$ .

$$\therefore \bar{V} = \bar{v}_R + \bar{v}_C$$

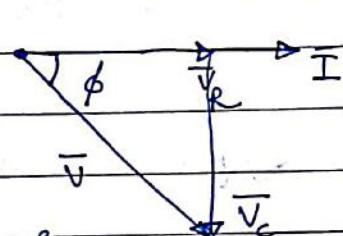phasor dia:- The current ( $I$ ) flows through the R & C. so, that  $I$  is taken as reference



fig(a):- phasor diagram

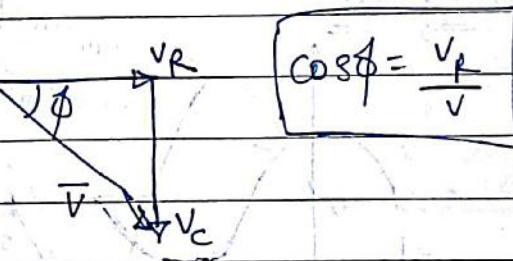

fig(b):- vfg. Triangle

Impedance:-

$$\bar{V} = \bar{v}_R + \bar{v}_C$$

$$= R \bar{I} - j X_C \bar{I}$$

$$\bar{V} = \bar{I} (R - j X_C)$$

$$\Rightarrow \frac{\bar{V}}{\bar{I}} = R - j X_C = \bar{Z}$$

$$\therefore \bar{Z} = Z \angle -\phi$$

$$\therefore Z = \sqrt{R^2 + X_C^2} = \sqrt{R^2 + \frac{1}{\omega^2 C^2}} \quad \& \quad \phi = \tan^{-1} \left( \frac{X_C}{R} \right)$$

$$\phi = \tan^{-1} \left( \frac{1}{\omega C R} \right)$$

where;  $\bar{Z}$  - is called complex impedance of series R-C Ckt.

Impedance Triangle:-

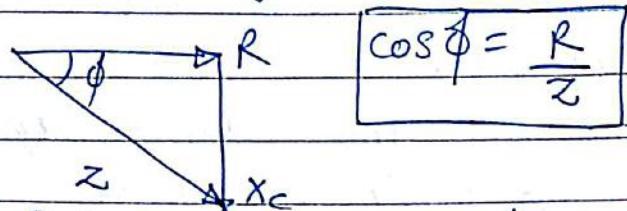


Fig:- Impedance triangle

Current:-

From the phasor diagram, it is clear that the current  $I$  leads the vfg ( $V$ ) by an angle  $\phi$ .

If the applied vfg is given by  $V = V_m \sin \omega t$  then the current will be;

$$I = I_m \sin(\omega t + \phi).$$

Where;  $I_m = \frac{V_m}{Z}$

$$\therefore \phi = \tan^{-1} \left( \frac{X_c}{R} \right) = \tan^{-1} \left( \frac{1}{\omega C R} \right)$$

Waveform:-

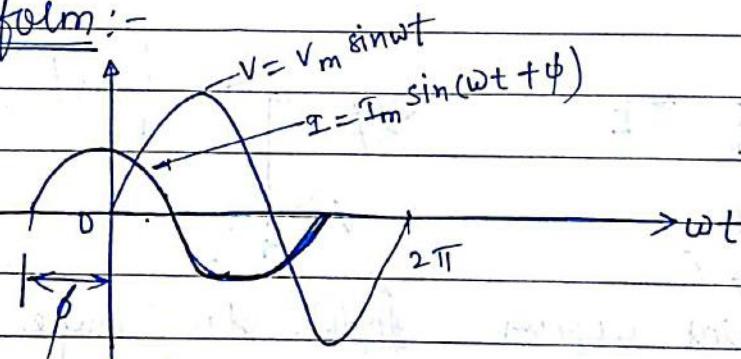


Fig:- waveform

Power:-

$$\text{Active Power (P)} = VI \cos \phi = I^2 R$$

$$\text{Reactive Power (Q)} = VI \sin \phi = I^2 X_c$$

$$\text{Apparent Power (S)} = VI = I^2 Z$$

Power triangle:-

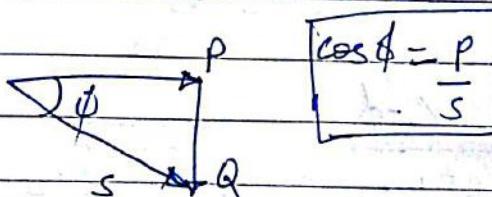


Fig:- power triangle

power factor:- It is defined as the angle between current & voltage phasors.

$$PF = \cos\phi$$

∴ from Vtg triangle;  $PF = \frac{VR}{V}$

from Impedance triangle;  $PF = \frac{R}{Z}$

from power triangle;  $PF = \frac{P}{S}$

In case of an R-C series ckt., the power factor is leading in nature.

Numericals:-

① An ac ckt. consists of a pure resistance of  $10\Omega$  & is connected across an ac supply of  $230V, 50Hz$ .

Calculate; ① current; ② power consumed; ③  $PF$ ;

④ write down the eqns for Vtg & current.

Sol:- Given data:-  $R = 10\Omega$

$$V = 230V$$

$$f = 50Hz$$

①  $CIN$   $I = \frac{V}{R} = \frac{230}{10} = 23 \text{ Amp}$

② power consumed  $P = VI = 230 \times 23 = 5290 \text{ watt}$

③  $PF = \cos\phi = \frac{P}{S}$  In case of pure R → angle betn Vtg & CIN is zero

$$\phi = 0$$

$$PF = \cos\phi = 1$$

④  $V_{rms} = \frac{V_m}{\sqrt{2}}$   $\Rightarrow V_m = \sqrt{2} V_{rms} = \sqrt{2} \times 230 = 325.27V$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \Rightarrow I_m = \sqrt{2} I_{rms} = \sqrt{2} \times 23 = 32.53 \text{ Amp.}$$

$$w = 2\pi f = 2\pi \times 50 = 100\pi = 314.16 \text{ rad/sec}$$

$$\therefore V = V_m \sin wt = 325.27 \sin(314.16 t)$$

$$I = I_m \sin wt = 32.53 \sin(314.16 t)$$

- ② An inductive coil having negligible resistance & 0.1 henry inductance is connected across 200V, 50 Hz supply. calculate; (i) inductive reactance; (ii) rms value of current; (iii) power; (iv) pf; (v) eqn for v & i

Soln:- Given data:-

$$L = 0.1 \text{ H}$$

$$V = 200 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$\text{(i) Inductive reactance } (X_L) = 2\pi f L = 2\pi \times 50 \times 0.1 \\ = 31.42 \Omega$$

$$\text{(ii) rms value of current } \Rightarrow I = \frac{V}{X_L} = \frac{200}{31.42} = 6.37 \text{ Amp}$$

(iii) power  $\Rightarrow$  since; the current is lags behind the vtg by  $90^\circ$ .

$$\therefore \phi = 90^\circ \quad \cos \phi = \cos(90^\circ) = 0$$

$$\therefore P = V I \cos \phi = 0 \quad \boxed{P=0}$$

$$\text{(iv) Power factor} \Rightarrow \boxed{\cos \phi = 0}$$

(v) Eqns of vtg & current :-

$$V_m = \sqrt{2} V_{rms} = \sqrt{2} \times 200 = 282.84 \text{ V}$$

$$I_m = \sqrt{2} I_{rms} = \sqrt{2} \times 6.37 = 9 \text{ Amp.}$$

$$\omega = 2\pi f = 2 \times 50 \times 3.14 = 314.16 \text{ rad/sec}$$

$$\therefore V = V_m \sin \omega t = 282.84 \sin(314.16 t)$$

$$\therefore I = I_m \sin(\omega t + \phi - \pi/2) = 9 \sin(314.16 t - \pi/2)$$

- ③ The vtg & current through ckt. elements are;

$$V = 100 \sin(314 t + 45^\circ) \text{ volt}$$

$$i = 10 \sin(314 t + 315^\circ) \text{ amp.}$$

(i) Identify the ckt. elements

(ii) find the value of elements

(iii) obtain an expression for power.

Sol:- Given data:-  $v = 100 \sin(314t + 45^\circ)$  —①

 $i = 10 \sin(314t + 315^\circ)$ 
 $= 10 \sin(314t + 315^\circ - 360^\circ)$ 
 $i = 10 \sin(314t - 45^\circ)$  —②

i) From eqn ① & ②; the angle i.e. phase difference is  $(-90^\circ)$  i.e. it is clear that the current (i) lags behind the Vfg by  $90^\circ$ . Hence; Gkt. element is an inductor

ii) Value of Element :-

$$X_L = \frac{V}{I} = \frac{V_m}{I_m} = \frac{100}{10} = 10 \Omega$$

$$X_L = \omega L$$

$$10 = 2\pi f L$$

$$L = \frac{10}{2\pi f} = \frac{10}{100\pi} = 31.8 \text{ mH}$$

$$L = 31.8 \text{ mH}$$

iii) Expression of Power :-

$$\therefore P = -\frac{V_m I_m}{2} \sin 2\omega t = -\frac{100 \times 10}{2} \sin(2 \times 314t)$$

$$\Rightarrow P = -500 \sin(2\omega t)$$

$$\Rightarrow P = -500 \sin 628t$$

## # Series Resonance :-

A circuit containing reactance is said to be in resonance if the V<sub>tg</sub> across the circuit is in phase with the current through it. At resonance, the circuit thus behaves as a pure resistor and the net reactance is zero.


Consider the series R-L-C circuit as shown in fig. ①

The Impedence of ckt is given by;

$$\therefore \bar{Z} = R + jX_L - jX_C$$

$$\Rightarrow \bar{Z} = R + j\omega L - j\frac{1}{\omega C}$$
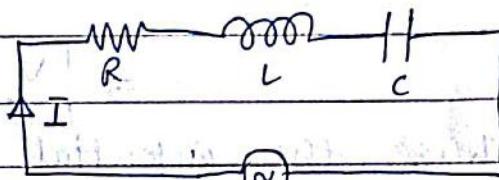
$$\Rightarrow \bar{Z} = R + j \left[ \omega L - \frac{1}{\omega C} \right]$$



$$V = V_m \sin \omega t$$

fig ① :- series RLC ckt.

At resonance,  $\bar{Z} = R$  i.e. resistive.

Therefore; the cond<sup>n</sup> for resonance is;

$$\omega L - \frac{1}{\omega C} = 0$$

$$\omega_0^2 LC - 1 = 0$$

$$\omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \quad \therefore \omega_0 = 2\pi f_0$$

$$\Rightarrow 2\pi f_0 = \frac{1}{\sqrt{LC}} \Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}}$$

where;  $f_0$  = Resonant frequency of the ckt.

power factor :- power factor =  $\cos \phi = R/Z$

But; at resonance;  $Z = R$

$$\therefore \cos \phi = \frac{R}{Z} = 1 \Rightarrow \cos \phi = 1$$

Current :- Since;  $Z$  is minimum, the current is max<sup>m</sup> at resonance. Thus, the ckt accepts more current and as such, an

R-L-C circuit under resonance is called an acceptor circuit.

$$I_0 = \frac{V}{Z} = \frac{V}{R}$$

Voltage:- At Resonance;  $\omega_0 L = \frac{1}{\omega_0 C}$

$$\Rightarrow \omega_0 L \cdot I_0 = \frac{1}{\omega_0 C} I_0$$

$$\Rightarrow V_{L_0} = V_{C_0}$$

Thus; the potential difference across Inductor is equal to potential difference across Capacitor being equal & opposite cancel each other.

Also;  $I_0$  - is max<sup>m</sup>

∴ hence;  $V_{L_0}$  &  $V_{C_0}$  - will be max<sup>m</sup>

Thus; the voltage magnification takes place during resonance. Hence; it is also referred to as vfg. magnification ckt.

phasor diagram:

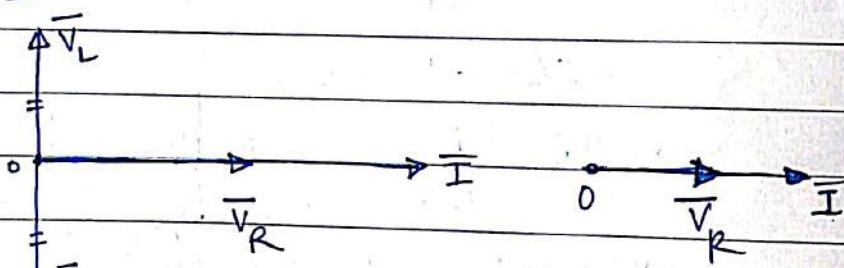


fig ②:- phasor dia

Behaviour of R, L & C with change in freq:-


∴ Resistance remains constant with change in frequencies.

∴ Inductive reactance ( $X_L$ ) is directly proportional to frequency ( $f$ ) ( $\therefore X_L = 2\pi f L$ )

∴ Capacitive reactance ( $X_C$ ) is inversely proportional to frequency ( $f$ ) ( $\therefore X_C = \frac{1}{2\pi f C}$ )

$\therefore X_L \propto f$  —  $\therefore$  It can be drawn as a straight line passing through origin.

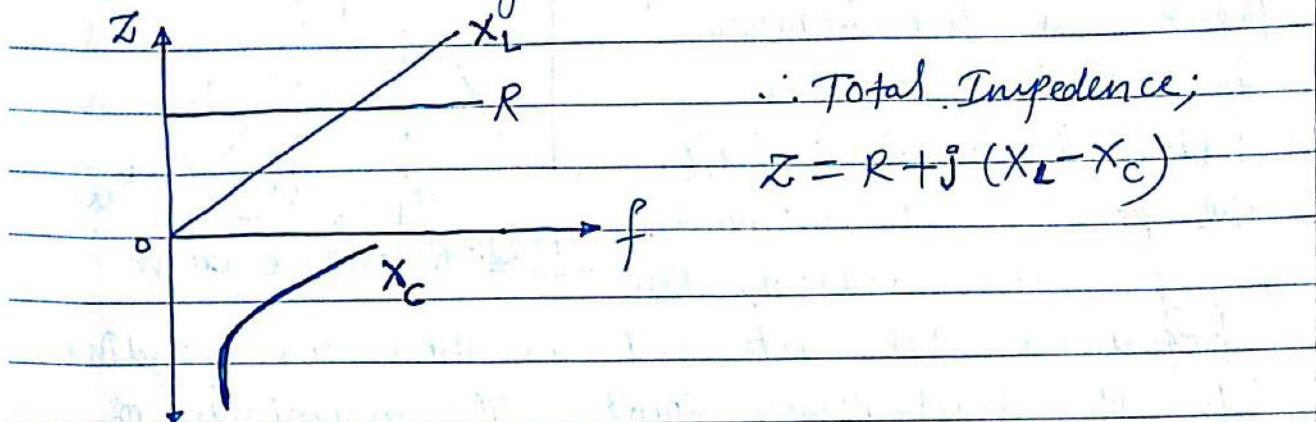$\therefore X_C \propto \frac{1}{f}$  —  $\therefore$  It can be drawn as a rectangular hyperbola in fourth quadrant.




fig(3): Behaviour of  $R, L$  &  $C$  with change in freq.

(a) When  $f < f_0$ , Impedance is capacitive and decreases up to  $f_0$ . The power factor is leading in nature.

(b) At  $f = f_0$ , Impedance is resistive. The power factor is unity.

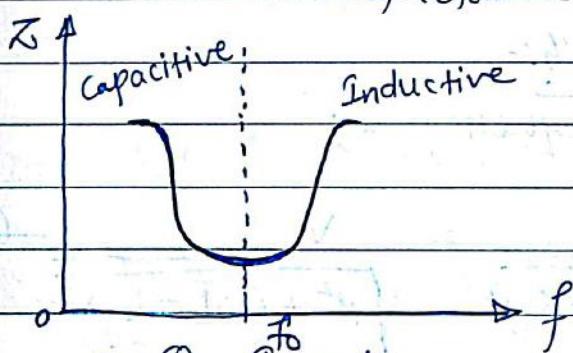(c) When  $f > f_0$ , Impedance is inductive & goes on increasing beyond  $f_0$ . The power factor is lagging in nature.



fig(4): Impedance

Bandwidth :- For series  $R-L-C$  ckt, bandwidth is defined as the range of frequencies for which the power delivered to  $R$  is greater than  $\frac{P_0}{2}$ .

where;  $P_0$  - is power delivered to  $R$  at resonance.

From the shape of curve; it is clear that there are two frequencies for which the power delivered to  $R$  is half the power at resonance.

fig 5:- Resonance curve

for this reason, these frequencies are referred as those corresponding to the half-power points. The magnitude of current at each half-power point is the same.

∴ Hence;

$$I_1^2 R = \frac{1}{2} I_0^2 R = I_2^2 R$$

Accordingly, the bandwidth may be identified on the resonance curve as the range of frequencies over which the magnitude of the current is equal to ~~or~~ greater than 0.707 of the current at resonance.

From fig. 5;

$$\text{The Bandwidth} = w_2 - w_1$$

Expression for Bandwidth:-


Generally; at any frequency  $w$ ;

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V}{\sqrt{R^2 + (wL - \frac{1}{wC})^2}} \quad \text{--- (1)}$$

∴ At half-power points;  $I = I_0/\sqrt{2}$

$$\text{But;} \quad I_0 = \frac{V}{R} \Rightarrow I = \frac{V}{\sqrt{2} \cdot R} \quad \text{--- (2)}$$
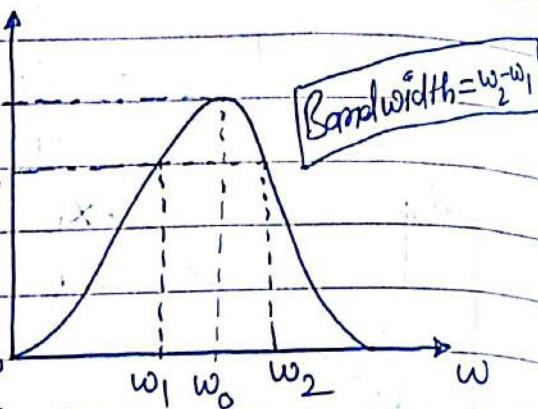
$$\text{from eqn (1) \& (2)} \Rightarrow \frac{V}{\sqrt{R^2 + (wL - \frac{1}{wC})^2}} = \frac{V}{\sqrt{2} \cdot R}$$



$$\Rightarrow \frac{1}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{1}{\sqrt{2} \cdot R}$$

$$\Rightarrow \sqrt{2} R = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$\therefore$  Squaring on b.s.

$$\therefore R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 = 2R^2$$

$$\Rightarrow \left(\omega L - \frac{1}{\omega C}\right)^2 = R^2$$

$$\Rightarrow \omega L - \frac{1}{\omega C} = \pm R$$

$$\Rightarrow \omega L - \frac{1}{\omega C} \pm R = 0 \quad \text{--- multiply by } (\omega C)$$

$$\Rightarrow \omega^2 LC - 1 \pm R \omega C = 0 \quad \text{--- divide by } \frac{1}{LC}$$

$$\Rightarrow \omega^2 - \frac{1}{LC} \pm \frac{R}{L} \omega = 0$$

$$\Rightarrow \omega^2 \pm \frac{2R}{2L} \omega - \frac{1}{LC} = 0$$

$$\Rightarrow \boxed{\omega = \pm \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}}$$

for low values of  $R$ , the term  $\left(\frac{R^2}{4L^2}\right)$  can be

neglected in comparison with the term  $\left(\frac{1}{LC}\right)$ .

$$\therefore \omega = \pm \frac{R}{2L} \pm \sqrt{\frac{1}{LC}}$$

$$\Rightarrow \boxed{\omega = \pm \frac{R}{2L} \pm \frac{1}{\sqrt{LC}}} \quad \text{--- } \textcircled{3}$$

Also;

The resonant freq. of ckt. is given by;

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}}} \quad \text{--- } \textcircled{4}$$

Substitute Equ<sup>n</sup> ④ in ③

$$\omega = \pm \frac{R}{2L} + \omega_0$$

Considering only  
+ve sign of  $\omega_0$ .

$$\therefore \omega_1 = \omega_0 - \frac{R}{2L} \Rightarrow f_1 = f_0 - \frac{R}{4\pi L}$$

$$\& \omega_2 = \omega_0 + \frac{R}{2L} \Rightarrow f_2 = f_0 + \frac{R}{4\pi L}$$

$$\therefore \text{Bandwidth} = \omega_2 - \omega_1 = \frac{R}{L}$$

$$\textcircled{m} \text{ Bandwidth} = f_2 - f_1 = \frac{R}{2\pi L}$$

Quality-factor :-

It is a measure of voltage magnification in series resonant ckt. It is also a measure of selectivity  $\textcircled{m}$  sharpness of the series resonant circuit.

$Q_0 = \frac{\text{voltage across inductor}}{\text{voltage at resonance}}$   $\textcircled{m}$  Capacitor

$$\Rightarrow Q_0 = \frac{V_{L0}}{V} = \frac{V_{C0}}{V}$$

Substituting values of  $V_{L0}$  and  $V$ ;

$$Q_0 = \frac{I_0 X_{L0}}{I_0 R} = \frac{X_{L0}}{R} = \frac{\omega_0 L}{R} \Rightarrow Q_0 = \frac{\omega_0 L}{R}$$

$$\textcircled{m} Q_0 = \frac{I_0 X_{C0}}{I_0 R} = \frac{X_{C0}}{R} = \frac{1}{\omega_0 RC} \Rightarrow Q_0 = \frac{1}{\omega_0 RC}$$

Substituting values of  $\omega_0$ ;

$$Q_0 = \frac{\frac{1}{\sqrt{LC}} L}{R}$$

$$\textcircled{m} Q_0 = \frac{\frac{1}{\sqrt{LC}} C}{R} = \frac{1}{\sqrt{\frac{C}{L}} R}$$

$$\Rightarrow Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\Rightarrow Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}}$$