

# JOIN



**Telegram**  
**@PuneEngineers**

**For more Subjects**

<https://www.studymedia.in/fe/notes>



 SCAN ME



Total No. of Questions : 8]

SEAT No. :

PA-4298

[Total No. of Pages : 4

[5924]-7

**F.E. (Electrical Engineering)**  
**BASIC ELECTRICAL ENGINEERING**  
**(2019 Pattern) (Semester - I/II) (103004)**

*Time : 2½ Hours]*

*[Max. Marks : 70*

*Instructions to the candidates:*

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.*
- 2) Figures to the right indicate full marks.*
- 3) Neat diagrams must be drawn wherever necessary.*
- 4) Assume suitable data wherever necessary.*
- 5) Use of non-programmable calculator is allowed.*

**Q1) a)** Calculate power factor angle and power factor in following cases : **[4]**

i)  $Z = 10 + j10 \Omega$

ii)  $Z = 30 - j20 \Omega$

b) If a single-phase AC supply is connected to RC circuit, answer the following. **[6]**

i) Draw circuit diagram indicating all voltage drop and current.

ii) Write equation for impedance and current.

iii) Draw the phasor diagram.

c) A coil of 100mH is connected in series with 25Ω resistance across 230V, 50 Hz supply. Find **[8]**

i) Inductive reactance and impedance

ii) Current through circuit

iii) Voltage drop across each element

iv) Active power

OR

*P.T.O.*

**Q2) a)** A sinusoidal voltage  $V = V_m \sin \omega t$  applied across pure resistance circuit. Derive expression active power consumed by the circuit. [4]

b) A pure capacitance of  $100\mu\text{F}$  is connected across single phase voltage given by  $v = 100 \sin (314t)$  volts. Find [6]

i) Frequency of supply in Hz

ii) Capacitive reactance

iii) Equation of current

c) A resistance  $20\Omega$ , inductance of  $50\text{mH}$  and capacitor of  $75\mu\text{F}$  are connected in series across  $230\text{V}$ , variable frequency supply. [8]

Calculate :

i) The frequency at which resonance will occur

ii) Current flowing through circuit

iii) Power factor

**Q3) a)** State the advantages of 3– ph system over 1-ph system (any 3) : [3]

b) What are the different losses in the transformer? In which party they take place and how to minimise them. [6]

c) A three phase load having per phase impedance  $(30 + j40)\Omega$  is connected in star across  $400\text{V}$ ,  $50\text{Hz}$ , 3-phase AC supply. [8]

Determine :

i) Line and phase voltage

ii) Line and phase current

iii) Power factor and power factor angle

iv) Active, reactive power

OR

**Q4) a)** State following statements are true or false with justification. [3]

i) In transformer, as the load current increases, iron losses increase.

ii) In transformer, as the load current increases, copper losses increase.

b) Derive emf equation of a single-phase transformer. [6]

c) Draw circuit diagram for delta load (RL types) connected across three phase balanced supply and derive relation between line and phase current and voltage. Also draw the phasor diagram. [8]

- Q5) a)** Define following terms : [4]
- i) Active and passive network
  - ii) Linear and non-linear network
- b)** Find the current following through  $2\Omega$  resistance using KVL. (Refer Fig. 5(b)) [6]

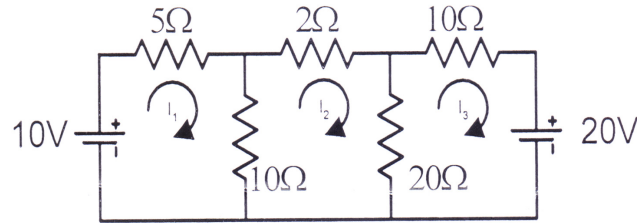


Figure 5b)

- c)** Determine equivalent resistance between XY Refer Fig. 5(c). [8]

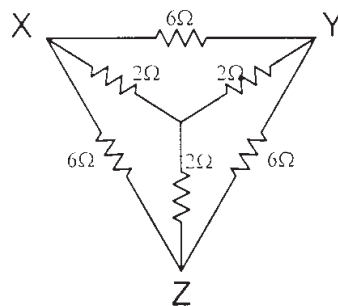


Figure Q5c)

OR

- Q6) a)** State and explain KCL and KVL. [4]
- b)**
- i) Three resistance each  $60\Omega$  are connected in delta, draw its equivalent star.
  - ii) Three resistance each  $60\Omega$  are connected in star, draw its equivalent delta.
- [6]
- c)** Write the steps to find current  $I_L$  in given circuit using Thevenin's theorem. [8]

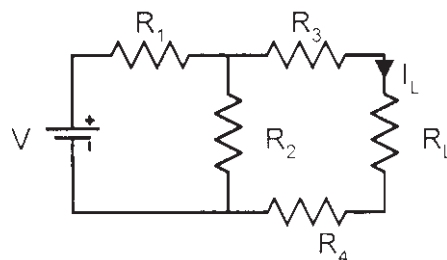


Fig Q6c)

**Q7) a)** State following statements are true or false with justification. [3]

- i) A wire is having resistance of  $10\Omega$ . If the length of wire is doubled, then new resistance is  $5\Omega$ .
- ii) A wire is having resistance of  $10\Omega$ . If the diameter of wire is doubled, then new resistance is  $2.5\Omega$ .

b) Explain construction, working of Lithium Ion Battery. [6]

c) Derive the formula for insulation resistance of a single core cable. State the factors affecting insulation resistance. [8]

OR

**Q8) a)** State the three conditions of fully charged lead acid battery. [3]

b) Explain construction, working and applications of Lead acid Battery. [6]

c) A wire is having resistance  $10\Omega$ ,  $20^\circ\text{C}$ , Its RTC at  $0^\circ\text{C}$  is  $0.004/^\circ\text{C}$ . Calculate :

- i) RTC at  $20^\circ\text{C}$
- ii) Resistance of wire at  $50^\circ\text{C}$
- iii) The temperature at which resistance increases to  $15\Omega$ .

